


Group 6:  
Sari Abu-Hamad  
Adarsh Chilkunda  
Drake Cote

## Workshop 1:

### Clock Dividers

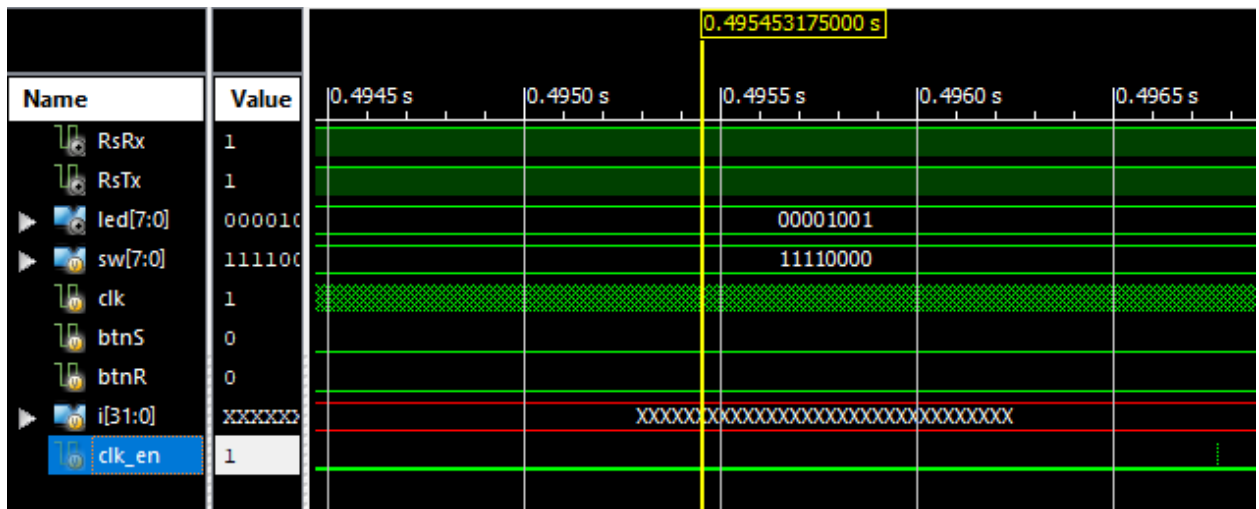1. Add `clk_en` to the simulation's waveform tab and then run the simulation again. Use the cursor to find the periodicity of this signal (you can select the signal and use arrow keys to reach the exact edges). Capture a waveform picture that shows two occurrences of `clk_en`, and include it in the lab report. Indicate the exact period of the signal in the report.

- Period:  $= 0.496763895000 - 0.495453175000 = 0.00131072$




2. A duty cycle is the percentage of one period in which a signal or system is active:  $D = T/P \times 100\%$ , where  $D$  is the duty cycle,  $T$  is the interval where the signal is high, and  $p$  is the period. What is the exact duty cycle of `clk_en` Signal?

- $0.496763905000 - 0.496763895000 = T = 1 \times 10^{-8}$
- $D = T/P \times 100\% = 1 \times 10^{-8} / 0.00131072 \times 100\% = 7.62939 \times 10^{-4}$

3. What is the value of `clk_dv` signal during the clock cycle that `clk_en` is high?

000000000000000000

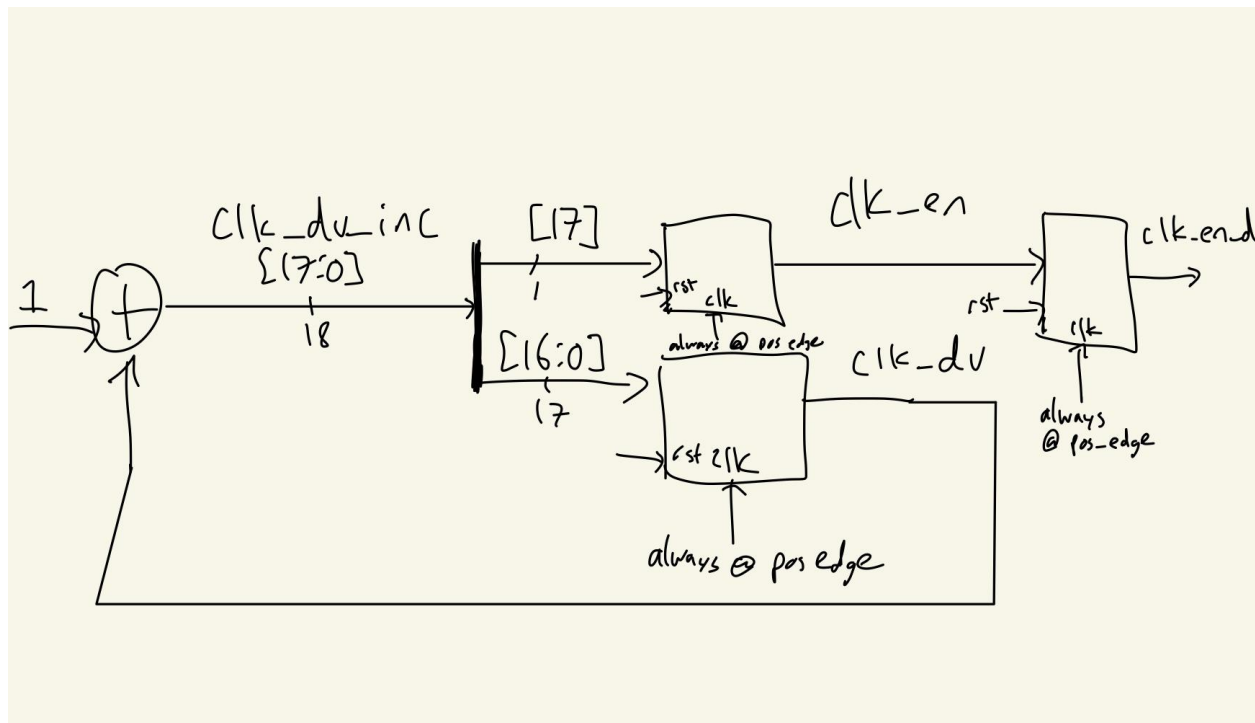4. Draw a simple schematic/diagram of signals `clk_dv`, `clk_en`, and `clk_en_d` signals. It should be a translation of the corresponding Verilog code



### Debouncing


1. What is the purpose of `clk_en_d` signal when used in expression `~step_d[0] & step_d[1] & clk_en_d`? Why don't we use `clk_en`?

The purpose of using the `clk_en_d` signal is to ensure `inst_vld` gets set to the correct value on the rising edge of the clock. If we set `inst_vld` to `clk_en`, it would read the wrong value because `clk_en` would not yet be high at the instant the clock goes high. Therefore, we use `clk_en_d` which stores the value of `clk_en` with a delay to ensure proper assignment.





2. Instead of `clk_en <= clk_dv_inc[17]`, can we do `clk_en <= clk_dv[16]`, making the duty cycle of `clk_en` 50%? Why?

Yes since `clk_dv_inc` is assigned to `clk_dv + 1`, and thus when `clk_dv` overflows, the highest bit of `clk_dv_inc` (17) will be 1. The next cycle, `clk_dv` will overflow to 0, so `clk_dv_inc` will be 0 + 1 = 1 and the highest bit will be 0. This allows `clk_en` to be on for one clock cycle period, making the duty cycle 50%.

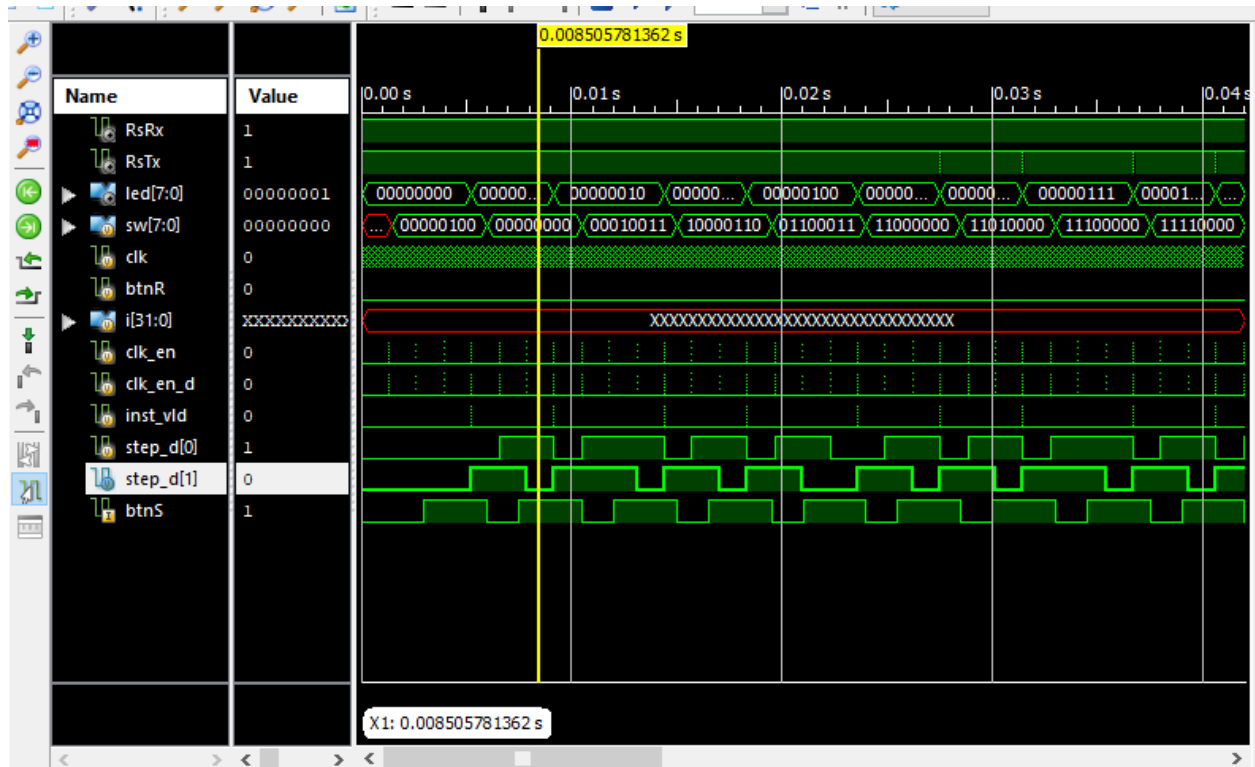3. Include waveform captures that clearly show the timing relationship between `clk_en`, `step_d[1]`, `step_d[0]`, `btnS`, `clk_en_d`, and `inst_vld`.



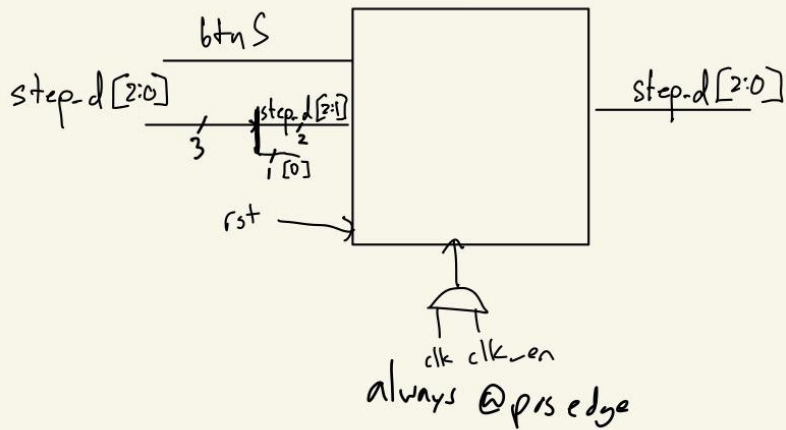  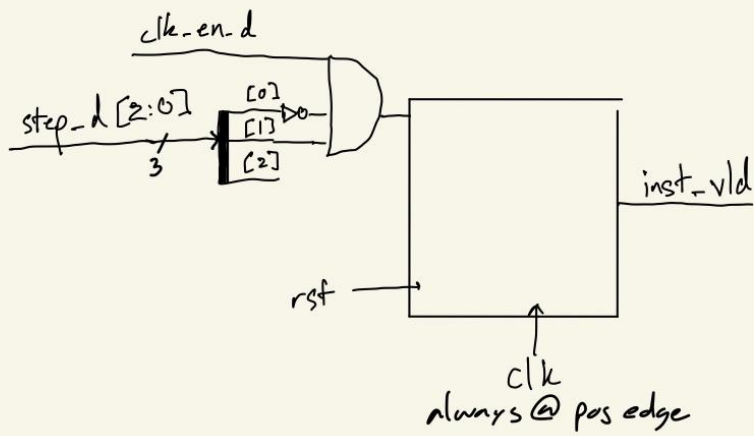4. Draw a simple schematic/diagram of the signals above. It should be a translation of the corresponding Verilog code.



## Register File


1. Find the line of code where a register is written a non-zero value. Is this sequential logic or combinatorial logic?

On line 33, register i\_wsel gets set to i\_wdata. This is sequential logic, because it is in an always @ (posedge clk) block. This only occurs when the clock is high.


2. Find the lines of code where the register values are read out from the register file. Is this sequential or combinatorial logic? If you were to manually implement the readout logic, what kind of logic elements would you use?

The register values are read out on lines 35 and 36. This is combinational logic (it's not in the always @ posedge clk block and so doesn't depend on clock signals). If we were to manually implement the readout logic, we would use wires since o\_data\_a and o\_data\_b are assigned the values in the register file. We would also use multiplexers to select the registers from the register file to be read out.

 3. Draw a circuit diagram of the register file block. It should be a translation of the corresponding Verilog code.



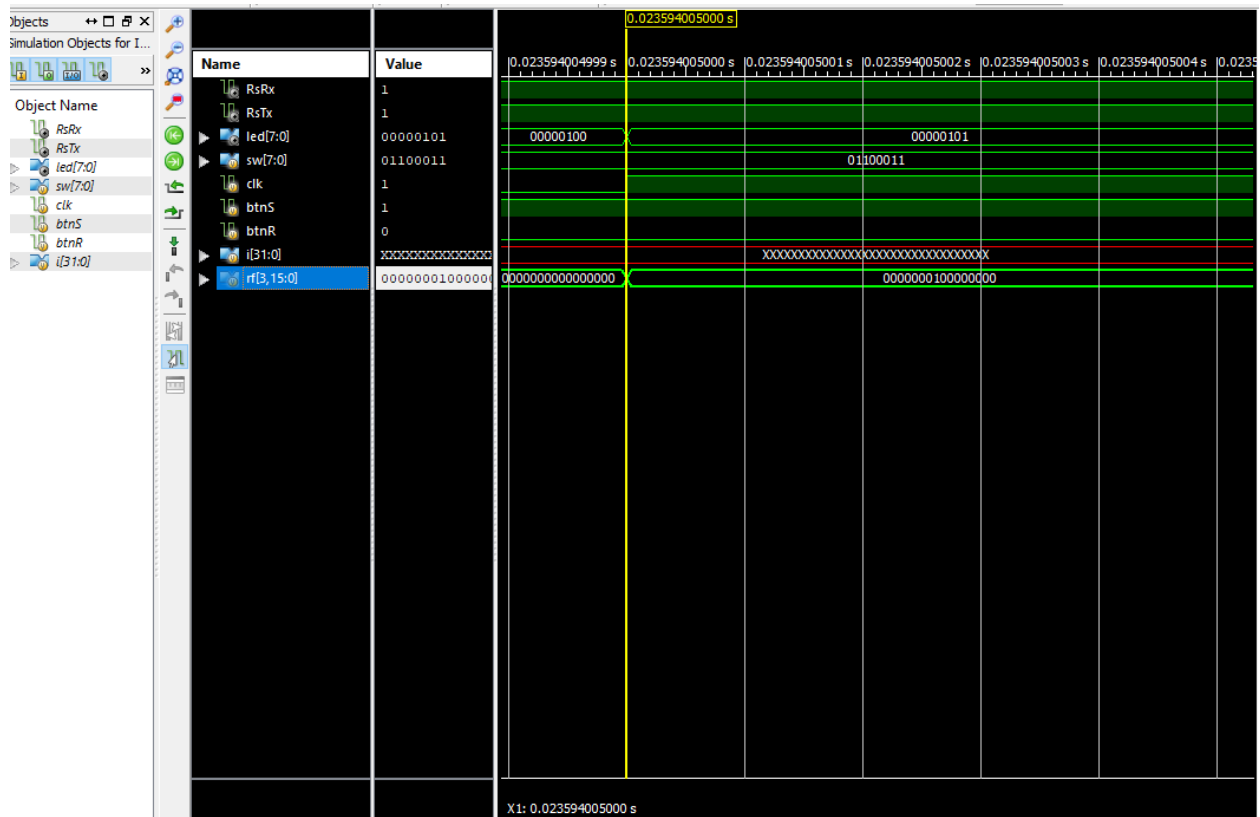4. Capture a waveform that shows the first time register 3 is written with a non-zero value.



## Workshop 2

1. Identify the part of the *tb.v* where the instructions are sent to the UUT.

The instructions are sent to the UUT in the “initial” block of *tb.v* after the #1500000 wait; this occurs on lines 29-41 for the source code where all of the *tskRun* tasks are run.

2. Which user tasks are called in this process?

The user tasks *tskRunPUSH*, *tskRunMULT*, *tskRunADD*, and *tskRunSEND* are called in this process in order to send specific instructions to the UUT.